



**FAMU-FSU**

**College of Engineering**



# **Towards a More General Model of Reversible Logic Hardware**

Invited talk presented Mar. 16<sup>th</sup>, 2012 at the *Superconducting Electronics Approaching the Landauer Limit and Reversibility (SEALeR)* workshop

**Michael P. Frank**

Dept. of Elec. & Comp. Eng., FAMU-FSU College of Engineering  
& Dept. of Physics, Florida A&M University




# A Simple Question

What is the simplest & most general universal set of primitive digital elements for implementing (adiabatic) reversible computing in CMOS?


A1: Fredkin gates (cSWAP)?

 \* Restricted to conservative logic (or dual-rail)




A2: Toffoli gates (ccNOT)?

 \* Still has six I/O terminals (3 input/3 output)



A3: cNOT?

 \* Simpler, but not universal w/o also quantum gates



Also, all the above elements consume all of their inputs, & emit an equal number of outputs each time they are applied...

Is that truly the most general framework?

A4: CMOS (nFET & pFET) transistors!



\* Instances of a more general class of elements for reversible computing.




# Transistors as Reversible Elements

- A (field-effect) transistor has 3 terminals only:
  - 1 input-only terminal (gate)
    - This input affects (but is not consumed by) the device
  - 2 bidirectional terminals (source/drain)
    - Generally these can act as inputs, or outputs, or both!
  - Actually, there is also a 4<sup>th</sup> (body) terminal
    - But we can ignore it for our present purposes
- Obviously, the operation of a transistor is not *always* reversible...
  - But, we'll see, it can be *conditionally* reversible
    - Under certain preconditions that we can define.
      - & this is sufficient for building any (classical) reversible digital computational functionality that we can imagine!


 
# High-Impedance (Z) States


- In general, a given physical I/O terminal between devices does *not* need to *always* be supplying a bias from one side to the other.
  - Another option: The terminal can be configured (on either, or both sides) as an open circuit.
    - No voltage sourced / no current sunk
- ‘Z’ states are frequently used in digital design!
  - Bidirectional I/O ports
  - Shared buses
  - Dynamic logic families, dynamic RAM




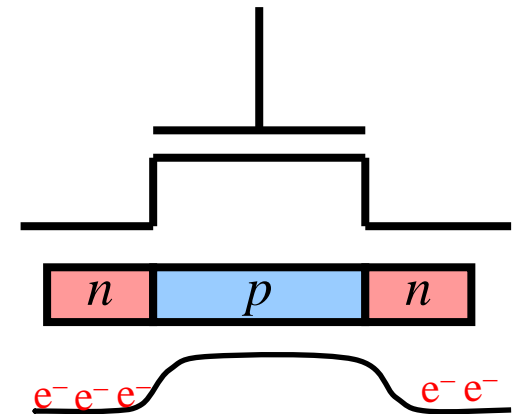
# FET Potential Energy Surface


- A FET provides a controllable potential energy surface for charge carriers, very similar to Landauer's bistable potential well model.
  - For an n-type FET:
    - Raise gate voltage  $\rightarrow$  lower potential energy barrier for electrons to pass between source and drain terminals.
      - In pFET: effect is opposite, and for holes
  - Apply bias voltage between source & drain terminals to “tilt” the potential energy surface
- Off transistor = open circuit
  - High- $Z$  terminal (as seen from either side)



# Possible Well Transitions


- Catalog of all the possible transitions in the bistable wells, **adiabatic** & **not**...
  - We can characterize a wide variety of digital logic and memory styles in terms of how their operation corresponds to subgraphs of this diagram.

(Ignoring superposition states.)

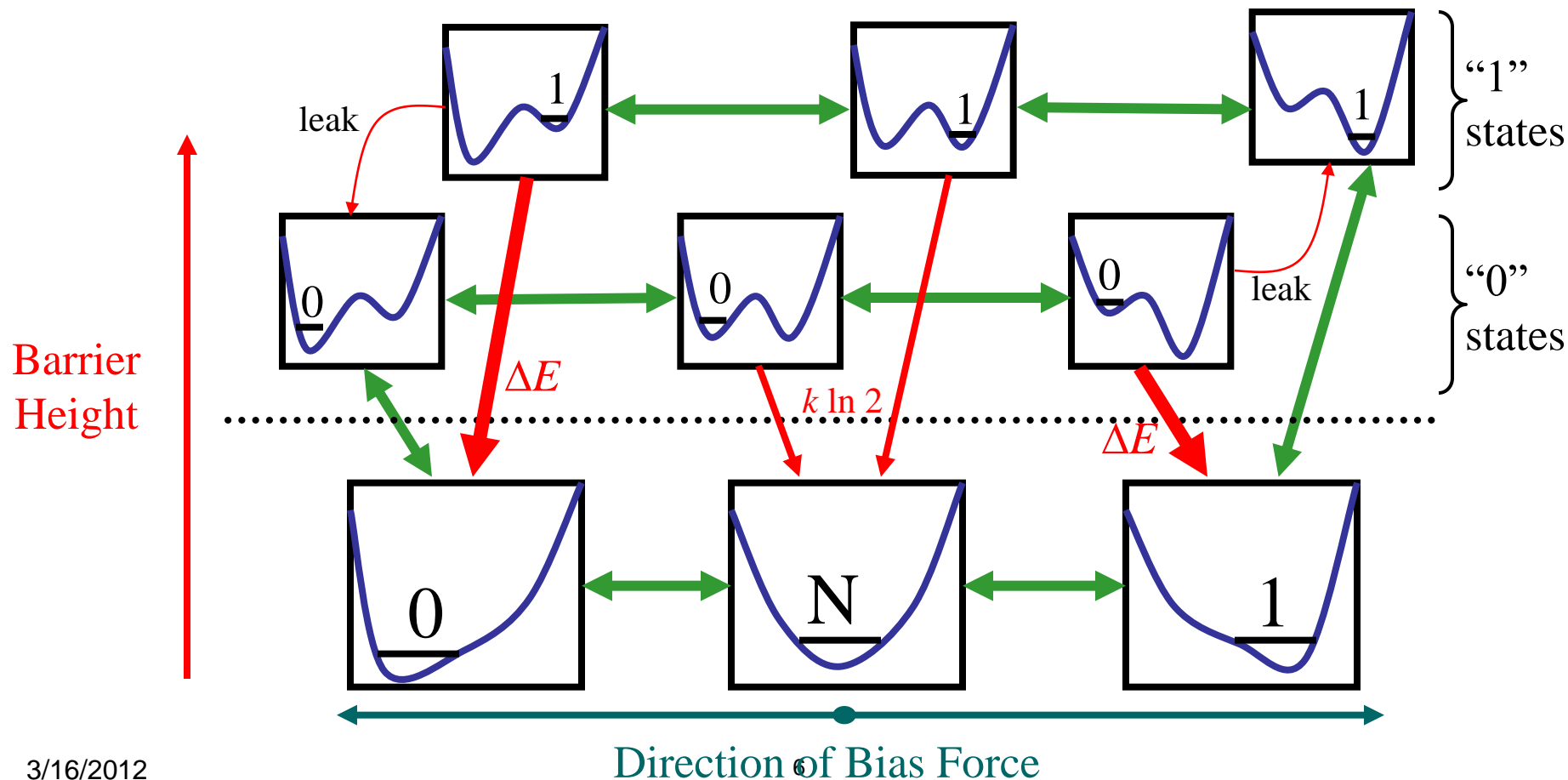
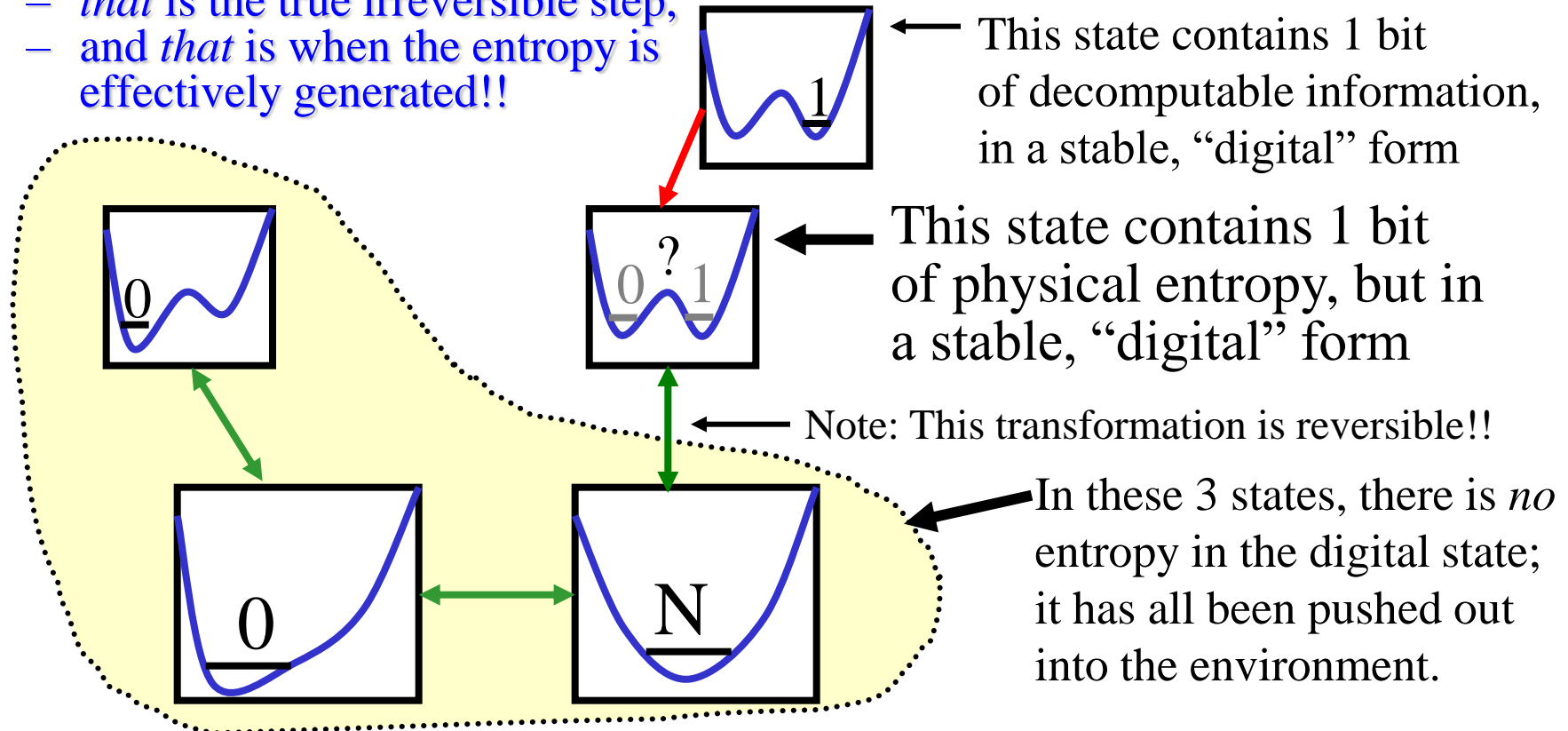
# Erasing Digital *Entropy*

- Note that if the information in a bit-system is *already* entropy,
  - Then erasing it just *moves* this entropy to the surroundings.
  - This can be done with a thermodynamically reversible process, and does *not* necessarily *increase* total entropy!
- However, if/when we take a bit that is known, and irrevocably commit ourselves to thereafter treating it as if it were *unknown*,
  - *that is* the true irreversible step,
  - and *that is* when the entropy is effectively generated!!





# Logic & Memory Styles

All describable within the potential-well paradigm!

- Irreversible styles:
  - *Input-barrier, constant-bias* logic.
    - *E.g.* standard static CMOS inverters & combinational gates.
  - *Input-bias, clocked-barrier* latching.
    - Standard static CMOS latches, dynamic RAM cells, *etc.*
- Reversible styles:
  - **Type 1:** *Input-bias, clocked-barrier* latching.
  - **Type 2:** *Input-barrier, clocked-bias* logic.
  - **Type 3:** *Input-barrier, clocked-bias* latching logic.
- All of these are available in a very wide variety of different physical instantiations of the bistable well.
  - *E.g.*, CMOS, superconducting, quantum-dot, Y-branch switches, mechanical implementations, *etc.*






# Rules for (Asymptotically) Reversible Operation of a FET


- **Rule 1:** Never turn *on* a transistor when there is a (non-negligible) *voltage* between source & drain terminals.
  - Leads to sudden order- $CV^2$  losses.
- **Rule 2:** (Obviously) never apply different biases simultaneously to source & drain of an “on” transistor.
  - Causes a (dissipative) short-circuit current across the device.
- **Rule 3:** Never change the voltage applied to any given terminal too rapidly (relative to  $RC$  of signal path)...
  - Especially to the source or drain of an “on” transistor!
    - Keeps the  $V_{DS}$  voltage drop (and the  $Q^2R/t$  losses) small
- **Rule 4:** Never turn *off* a transistor when there is a (non-negligible) *current* between source & drain terminals.
  - Exception: If there’s an alternate path between the same nodes!
  - Several early “adiabatic” logic families unwittingly failed to obey this rule → not truly/fully adiabatic!


 
# Finding Safe Adiabatic Transitions


- Given a set of logic levels,
  - And linear ramps between them,
- We can determine which combinations of gate/source/drain transitions are adiabatic.
  - Made easier because level-crossings can only occur at certain discrete times.
- A discrete circuit simulator was developed at UF that checks arbitrary 3-level circuits for full adiabaticity.



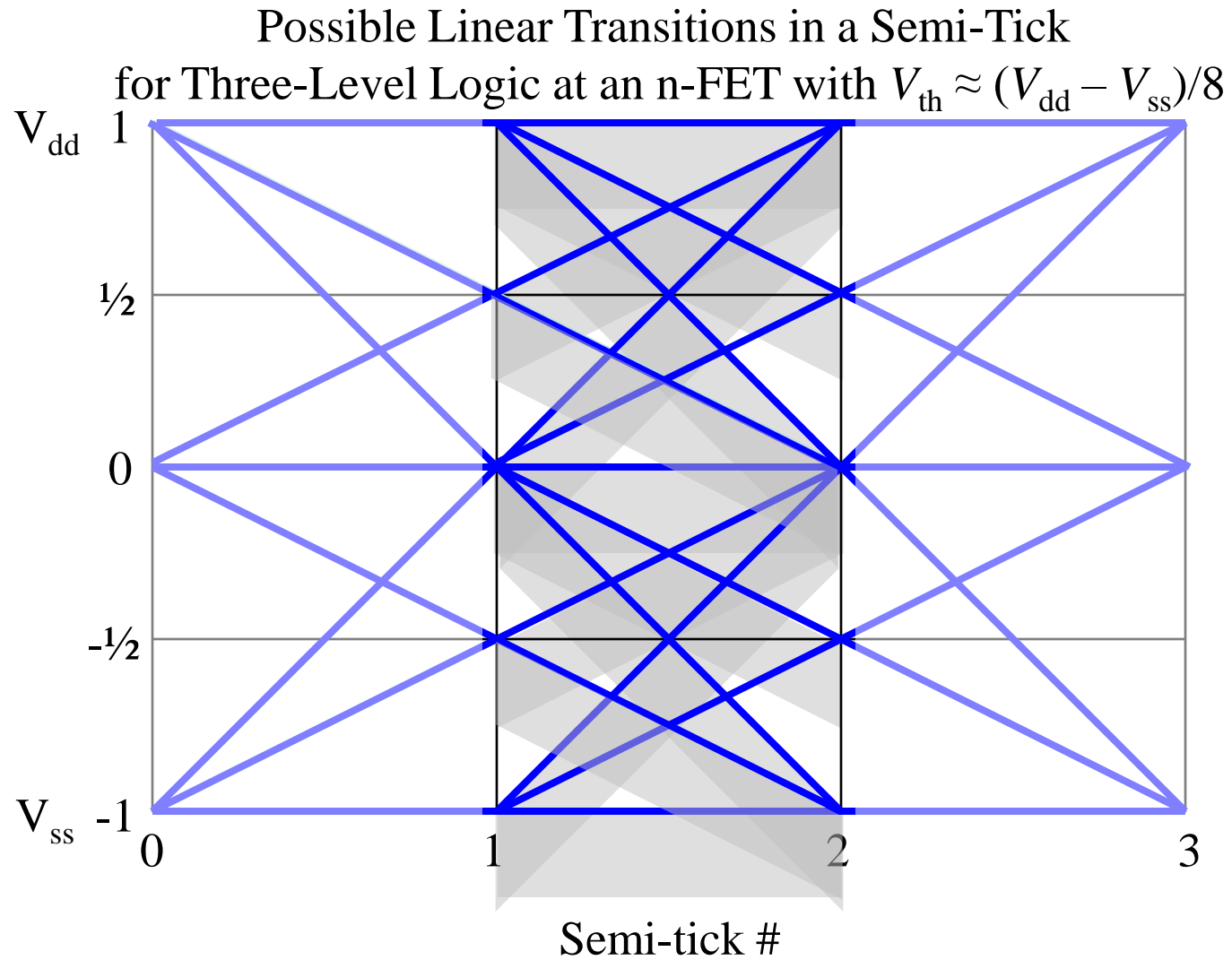



 
## Examples of Adiabatic Transitions: Example #1



(Always adiabatic – Source & drain remain connected throughout transition)



 
## Examples of Adiabatic Transitions: Example #2



(Always adiabatic – Source & drain become disconnected, but only while  $I_{DS} = 0$ )



 
### Examples of Adiabatic Transitions: Example #3



(Possibly adiabatic – But only if source & drain are *separately* being driven along identical trajectories)



 
## Examples of Adiabatic Transitions: Example #3



(Always adiabatic – Source & drain disconnected throughout transition)


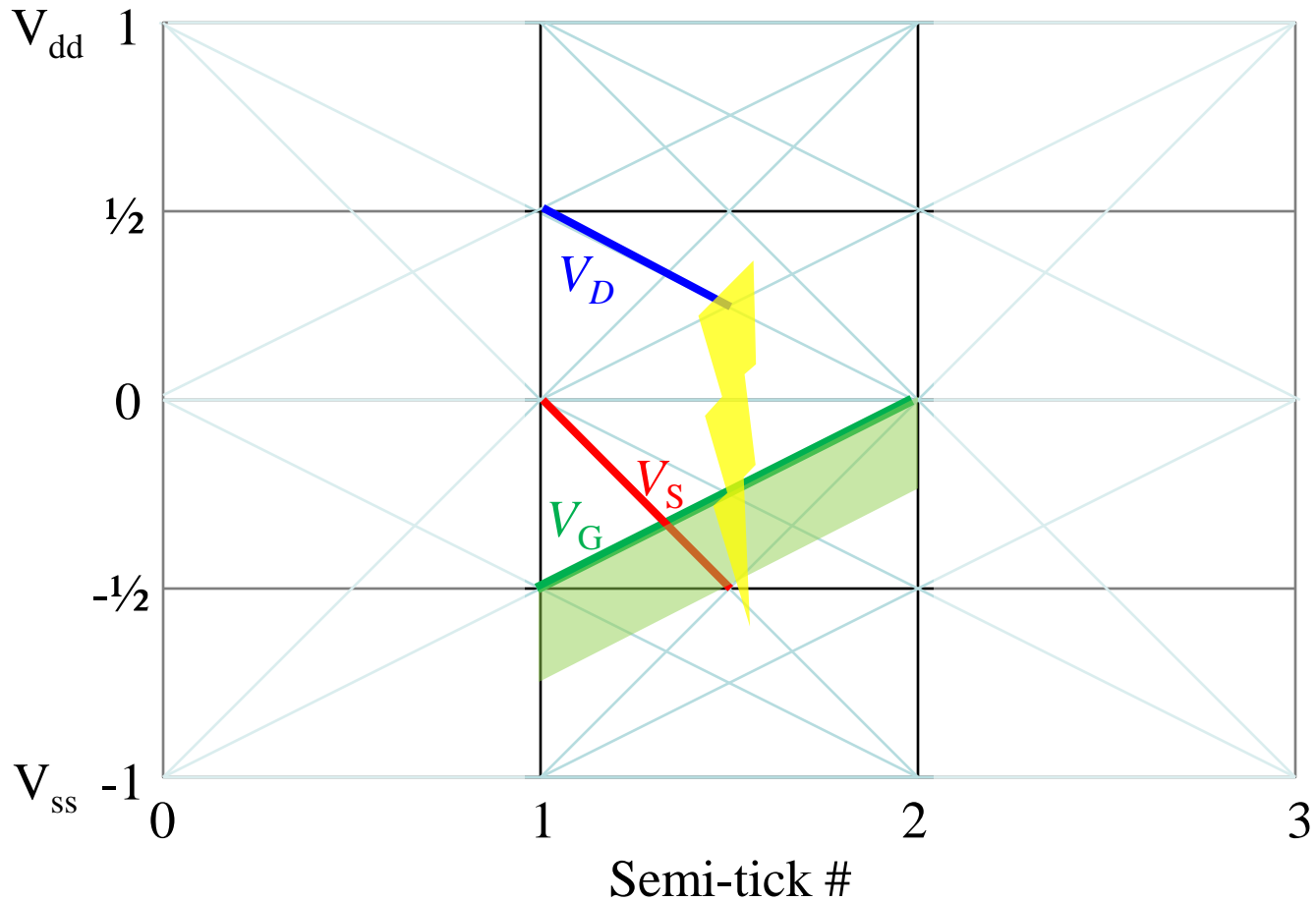
## Examples of **Non-Adiabatic** Transitions: Example #1




(Never adiabatic – Transistor turns on when  $V_{DS} \neq 0$ )




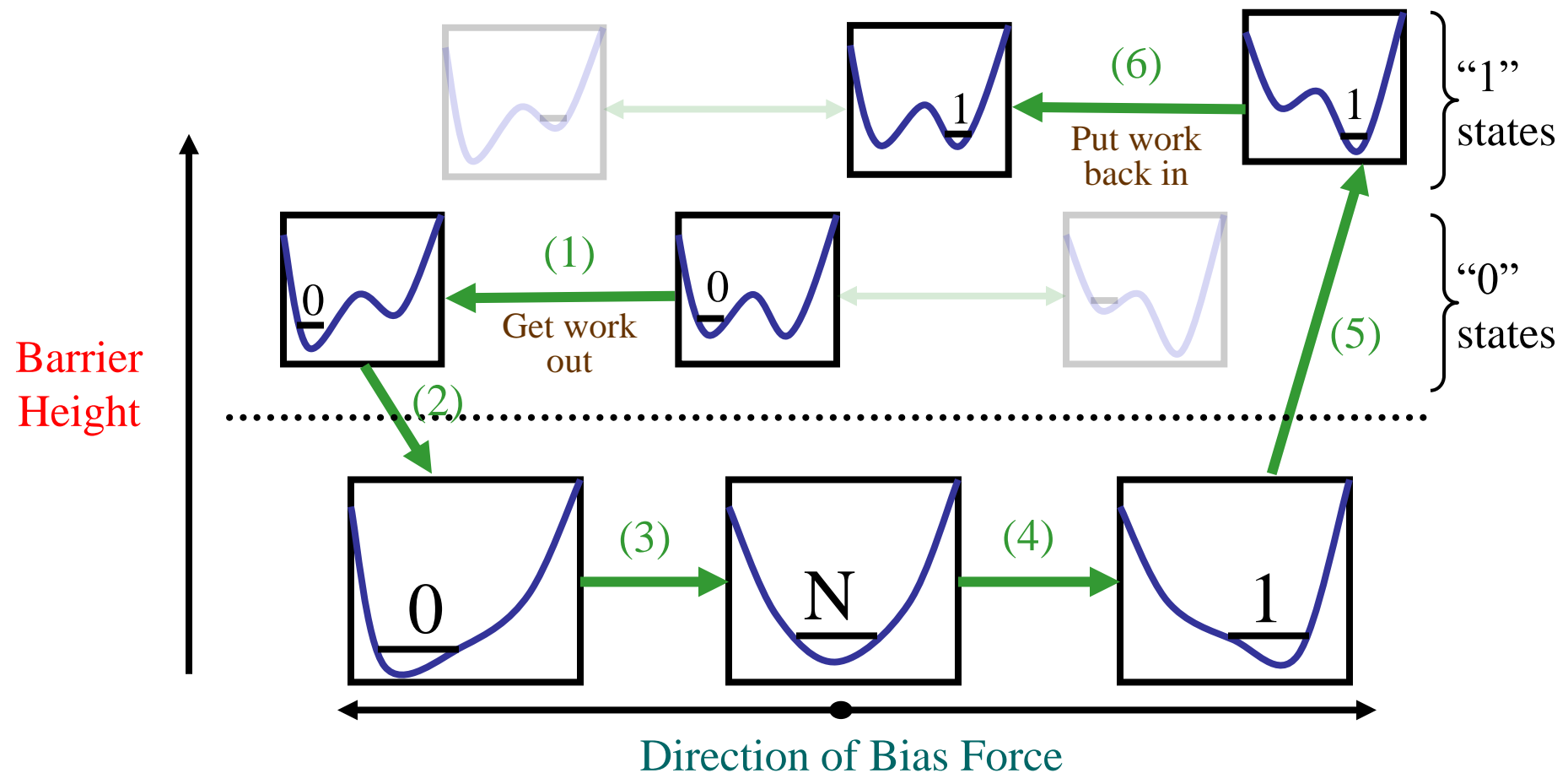
# Reversible Set (rSET) & Clear (rCLR)


- **rSET** operation semantics: Given assurance that a bit is initially 0, unconditionally change it to 1.
  - To implement: Traverse the adiabat (reversible trajectory) shown below.
- Reverse this path to perform **rCLR**.




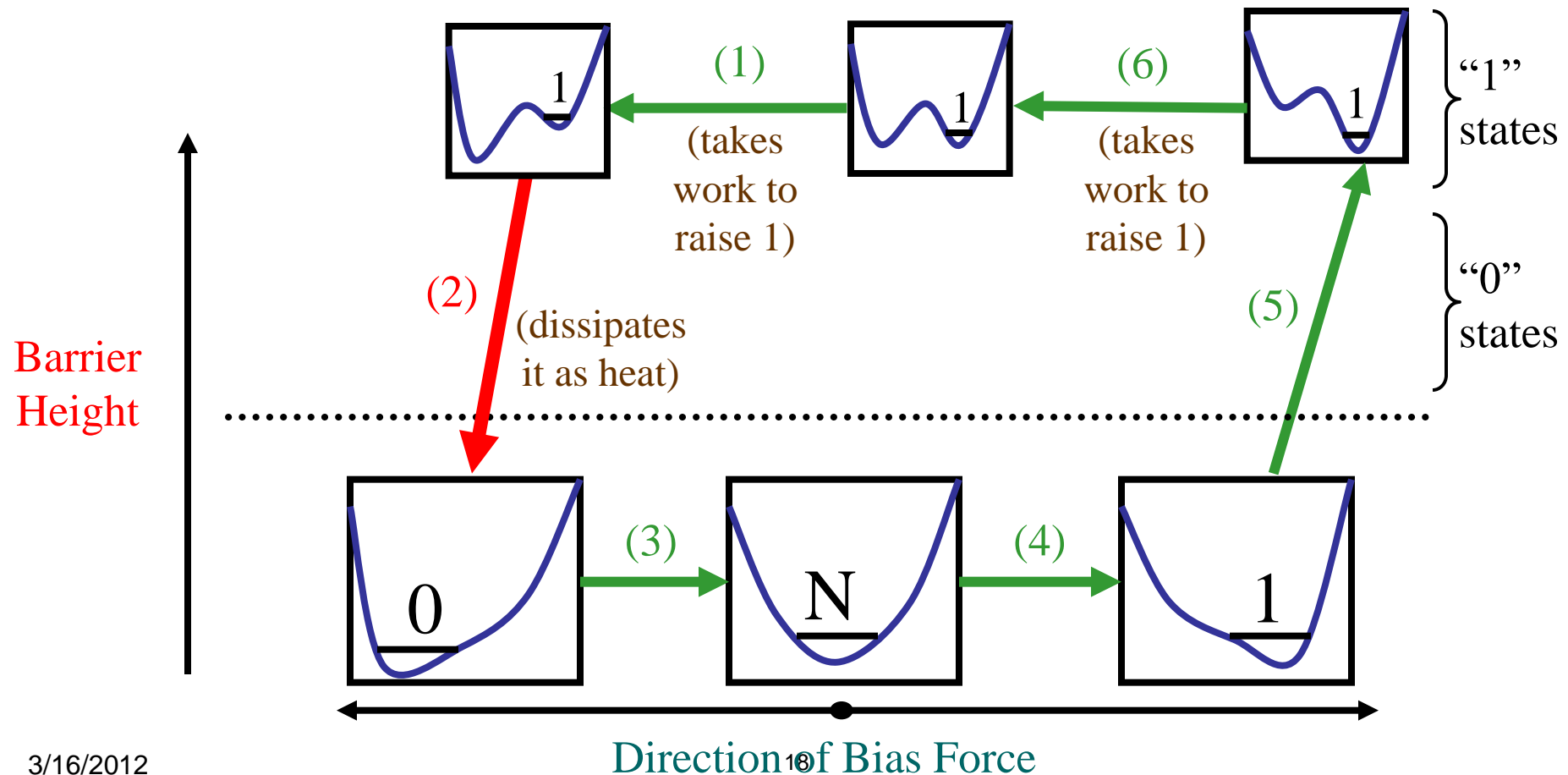
# Taking $rSET/rCLR$ out of context

- What happens if we attempt to perform  $rSET$  on a bit that is already a 1?
  - It still ends up with the right value (1), but...
  - Irreversible dissipation occurs in step 2 (when barrier is lowered), as shown below.
- Similarly if we try to  $rCLR$  a 0.





# rSET/rCLR transition tables

- Note that these tables are *not* logically reversible (invertible) according to the strict traditional definition...
  - Since they don't represent a one-to-one transformation of *all* possible initial states. (Some final states have >1 predecessor.)
- *However*, if we restrict our use of these operations so as to always *avoid* the input states that actually result in dissipation,
  - *Then*, we obtain a one-to-one transformation of *the subset of the possible initial states that are actually used* in the design,
  - And that is the correct statement of the minimum logical requirement for avoiding Landauer's limit!


Before rSET	After rSET
0	1
1	

Before rCLR	After rCLR
0	
1	0


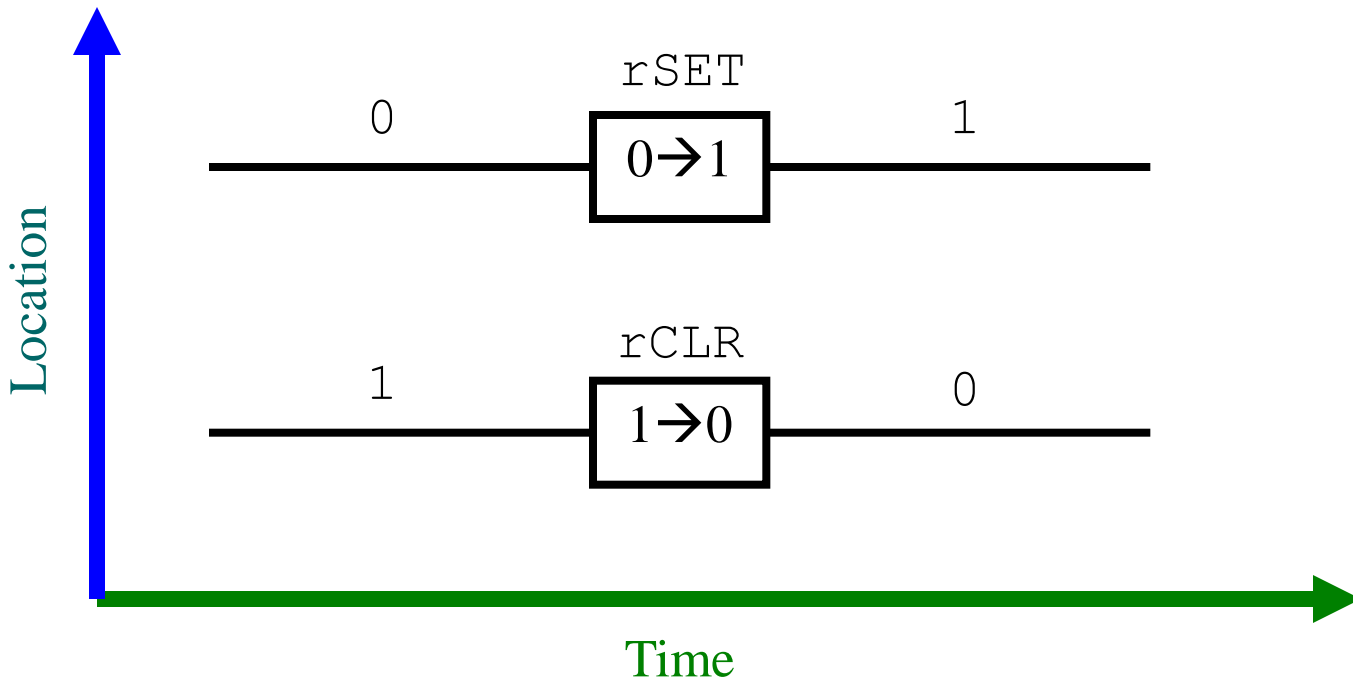
# rSET/rCLR in spacetime diagram

- Here is a suggested graphical notation for rSET/rCLR in the spacetime diagram picture.
  - However, keep in mind that the spacetime diagram formalism omits representation of the control signal that determines exactly *when* the operation occurs.





# Type 1: Input-Bias Clocked-Barrier Reversible Latching (& Logic)

## • Cycle of operation:

– (1) Data input applies bias


(Can amplify/restore input signal in the barrier-raising step.)

• Add forces to do majority logic

– (2) Clock signal raises barrier

– (3) Data input bias removed

 Can reset latch reversibly (4) given copy of contents.




**Examples:** Adiabatic QCA, SCRL latch, Rod logic latch, PQ logic, Buckled logic, Helical logic


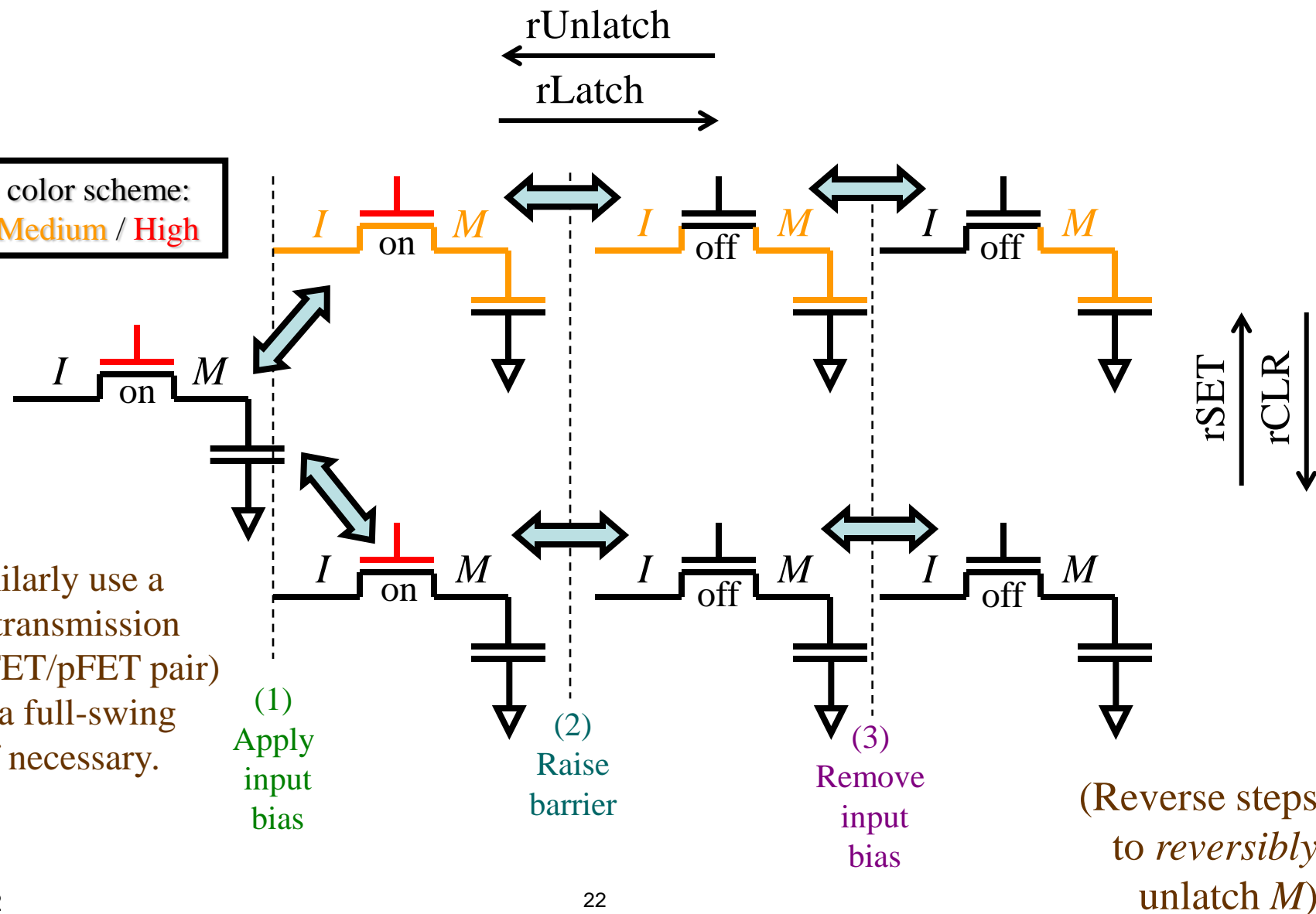
# 1-transistor Adiabatic rSET/rCLR/latch/DRAM cell

Voltage color scheme:  
**Low** / **Medium** / **High**




Can similarly use a CMOS transmission gate (nFET/pFET pair) to latch a full-swing signal if necessary.


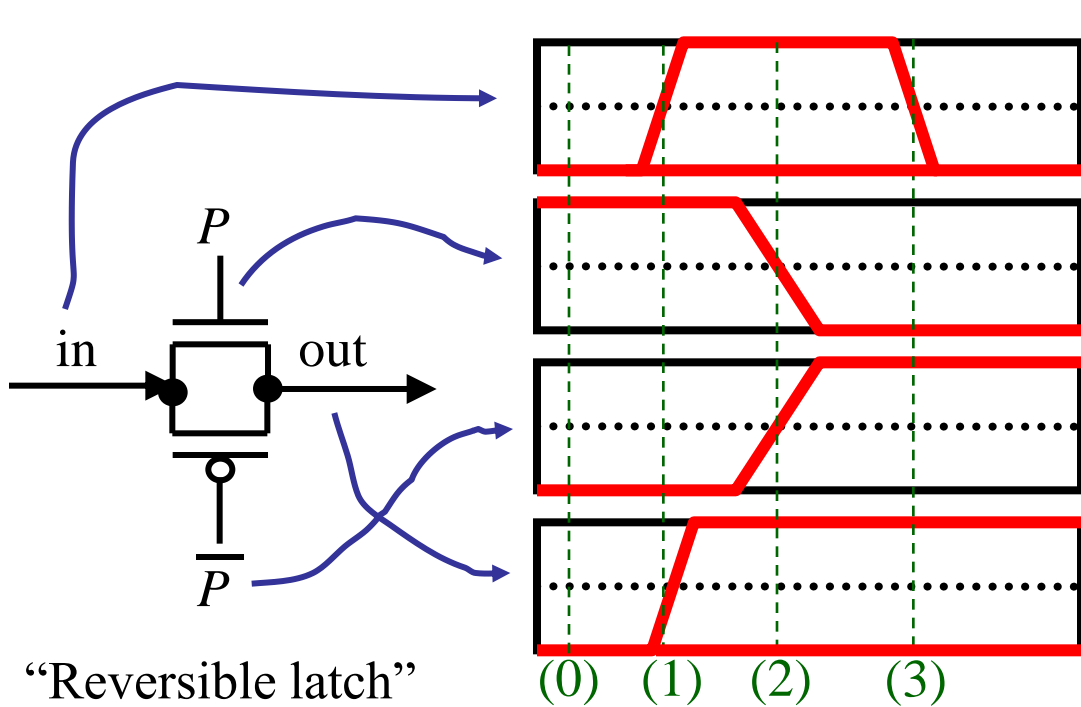
# A Simple Reversible CMOS Latch

- Uses a single standard CMOS *transmission gate* (T-gate).
- Sequence of operation:
  - (0) input level initially tied to latch 'contents' (output);
  - (1) input changes gradually → output follows closely;
  - (2) latch closes, charge is stored dynamically (node floats);
  - (3) afterwards, the input signal can be removed.




Before input:		Input arrived:		Input removed:	
<u>in</u>	<u>out</u>	<u>in</u>	<u>out</u>	<u>in</u>	<u>out</u>
0	0	0	0	0	0
		1	1	0	1

- Later, we can reversibly “unlatch” the data with an exactly time-reversed sequence of steps.




# Reversible latch in spacetime diagram

## diagram

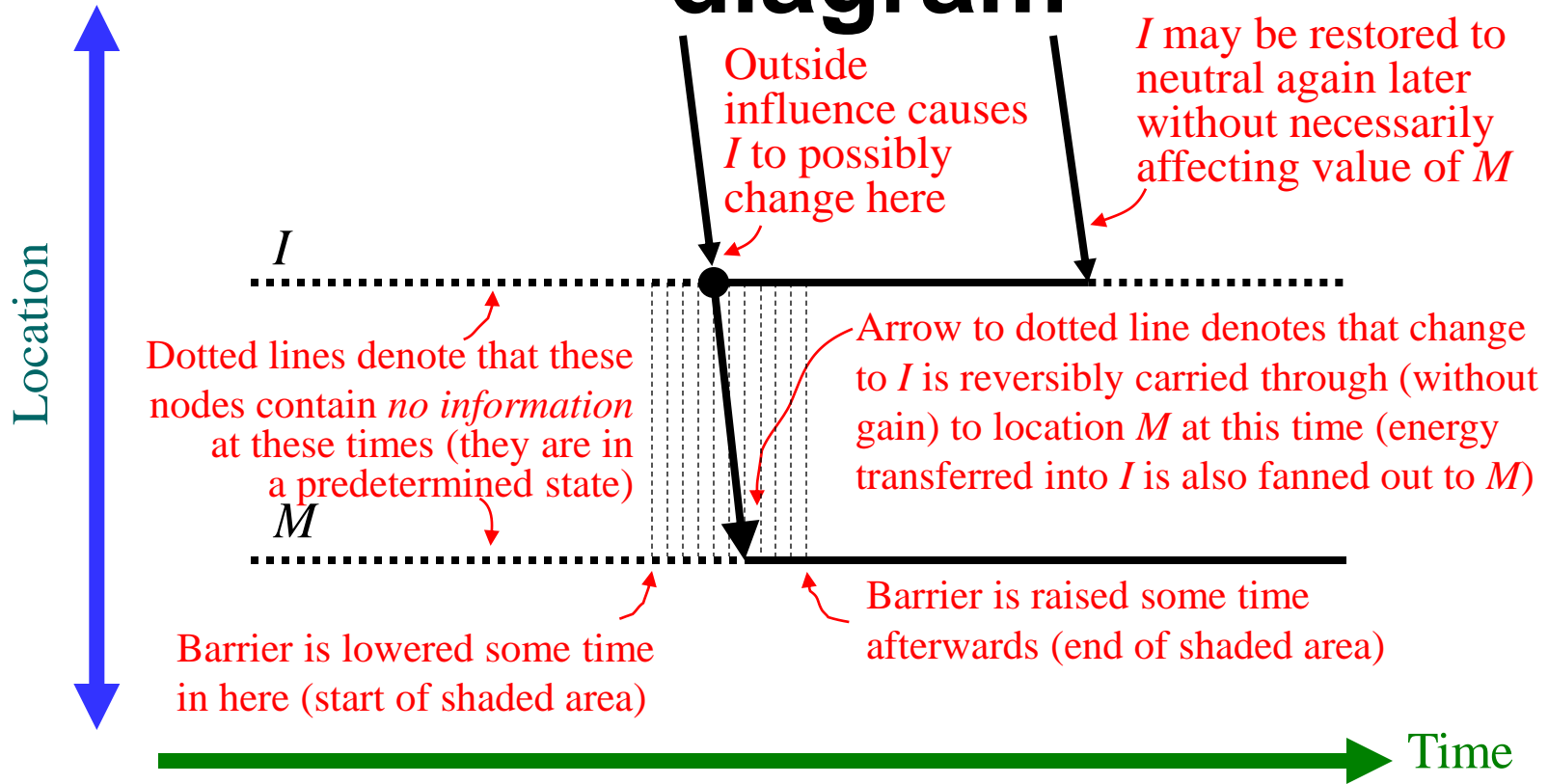

Unlatching sequence:

 


Note this operation is adiabatic only if  $I$  and  $M$  match up exactly when they are first connected together!




 
# Icon for Latch


- Extremely simple notation:
  - Just draw a short orthogonal line across the wire to indicate the presence of a latch at that point.
    - Control of latch timing is implicit.



- Note the same latch hardware can actually be used to latch signals being passed in either direction. → It's symmetric in space and time.
 
# rCOPY - Spacetime Diagram

- Suppose the signal on the input node  $I$  was produced as a temporary copy of some origin node  $O$ .
  - We will see how to implement this reversibly later.
- Then for simplicity of our diagrams, we may wish to omit explicit representation of the intermediate node  $I$ .
  - However, we must keep in mind that there is then a small additional space usage not explicitly shown in the diagram.



# Operation Naming Conventions

- Clarification of our naming conventions for operations:

## **r** – “reversible”

- Means operation is a conditionally-reversible variant of an operation that would traditionally have been irreversible.

## **l** – “latching”

- Operation includes latching of result; *i.e.*, input operands aren't required to be held after output operand is modified.

## **c** – “controlled”

- First operand is a “control” input; operation is only performed if it is a 1.

## **Un** – “undo”

- Operation does the time-reversal of the operation without the “Un” prefix.

# Operations Encountered So Far

- Ordinary irreversible operations:
  - CLR( $a$ ):  $a := 0$ . Clear operation.
  - Invert( $a, b$ ):  $b := \underline{a}$ . Inverter operation.
  - AND( $a, b, c$ ):  $c := ab$ . AND gate operation.
  - OR( $a, b, c$ ):  $c := a+b$ . OR gate operation.
  - XOR( $a, b, c$ ):  $c := a \oplus b$ . XOR gate operation.
- Unconditionally reversible operations:
  - NOT( $a$ ):  $a := \underline{a}$ . In-place NOT operation.
  - cNOT( $a, b$ ):  $b := a \oplus b$ . Controlled-NOT operation.
  - ccNOT( $a, b, c$ ):  $c := ab \oplus c$ . Toffoli gate operation.
  - SWAP( $a, b$ ):  $a \leftrightarrow b$ . Swap operation.
  - cSWAP( $a, b$ ): if  $a, a \leftrightarrow b$ . Fredkin gate operation.
- Conditionally reversible operations:
  - rCLR( $a$ ): ( $a$ )  $a := 0$ . Reversible clear operation.
  - rcSET( $a, b$ ): ( $\underline{a} + \underline{b}$ ) if  $a, b := 1$ . Controlled rSET operation.
  - rCOPY( $a, b$ ): ( $\underline{b}$ )  $b := a$ . Reversible copy operation.

# Type 2: Input-Barrier, Clocked-Bias Reversible Retractable Logic


- **Cycle of operation:**

- (1) **Inputs raise or lower barriers**


- Do logic w. series/parallel barriers

 - (2) Clock applies bias force, which changes state, or not

- Barrier signal is amplified!  
Gain, restoring logic, fan-out.
- Must reset output prior to changing input.
- Combinational logic only!



(1) Input barrier height

 


(2) Clocked bias force applied →

## Examples:

Hall's logic,  
SCRL gates,  
Rod logic interlocks
 
# Type 2 example: Adiabatic CMOS “buffer” (really, a cSET/cCLR gate)

- Controlled-SET / controlled-CLEAR.
  - Using dual-rail signaling, we can reversibly set or clear a bit on an unoccupied logic node (pair of voltage nodes),
    - conditionally on an input node.
- Structure: Two CMOS transmission gates
  - 2 transistors each;
  - 4T total
- Features:
  - Amplifies input signal.
  - Fully restores logic levels.



(And similarly for  $Out_P$ )


# Transition Table for **cSET**

- It is not *always reversible*,
  - Not a one-to-one transformation of *all* possible local states,
- But, it is *conditionally reversible*
  - *I.e.*, on condition that input state 1,1 is avoided.
- Transition table for **cCLR** is similar.

Before <b>cSET</b>		After <b>cSET</b>	
Source	Destination	Source	Destination
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0
 
# Icon for **cSET/cCLR** gate

- Represents a gate that can perform either **cSET** or **cCLR** on the *Out* node, with either operation conditioned on  $In_{NP}$  being a logic 1.




- Constraints on use (in simple CMOS impl.):
  - Input must be a dual-rail pair.
  - The *Drive* control signal must have the same bus width as the *Out* signal.


 
# Spacetime diagram for buffer


- Subscript  $_{NP}$  notation denotes shorthand for dual-rail NP pair of wires.
  - Still denotes a single *logical* bit.
- Diagram emphasizes that the buffer copies  $In_{NP}$ 's value to a *new* location.
  - The value simultaneously remains available in the old location.
- Dotted horizontal line shows that  $Out_{NP}$  is empty prior to the operation.
  - The absence of “×” icon shows that the operation is reversible.
- Buffer icon indicates that the input signal is being amplified and restored.
  - Note that the input comes from  $In_{NP}$ , *not* from previous value of  $Out_{NP}$ .
- Downward wedges remind us the output remains dependent on the input.
  - Input can't be changed without (possibly) irreversibly destroying output.
- Fortunately, the buffer's entire operation sequence is reversible!
  - So, sometime later on, we can *unbuffer* the output,
    - and then we are free to change the input.



 
# Reversible Buffered Latch

- Uses two dual-rail T-gates.
- Combines a buffer and latch.
  - Reversibly copies  $In_{NP}$  to  $Mem_{NP}$  when operated.


This is our icon for a CMOS transmission gate (T-gate). It says that nodes  $A$  and  $B$  are connected whenever the control signal  $C_{NP}$  has logic value 1.




## Physical structure:

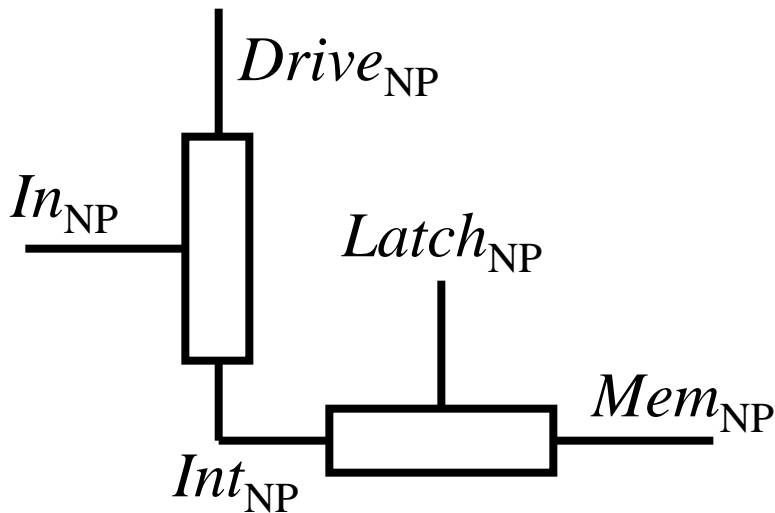
 
## Spacetime diagram for operation sequence:




## Implements “reversible copy”:

 
 
# Hardware Icon for Buffered Latch




- Looks a little bit like a diode icon, but isn't.
- Composed of our previous icons for:
  - Reversible buffer
  - Reversible latch



- This gate properly implements the **rlcSET**(*in,out*) and **rlcCLR**(*in,out*) operations!
  - The buffer alone does not quite do it, because of the constraint that *in* must be stable while *out* is driven.

   
# Three Ways to Use a Transmission Gate Reversibly

- **rSET/rCLR** – Drive signal and gate signals are both considered to be control.
  - Unconditional, not data-dependent.
- **rLatch/rUnlatch** – Drive signal is a data input, gate signals are control.
  - **rLatch(*in*,*out*)** just isolates *in* from *out*
- **cSET/cCLR** – Drive signal is a control signal, gate signals comprise data input.
  - **cSET(*in*,*out*)** presents a copy of *in* on *out*
- What if everything is a data input?
  - Some data transitions are reversible, others not


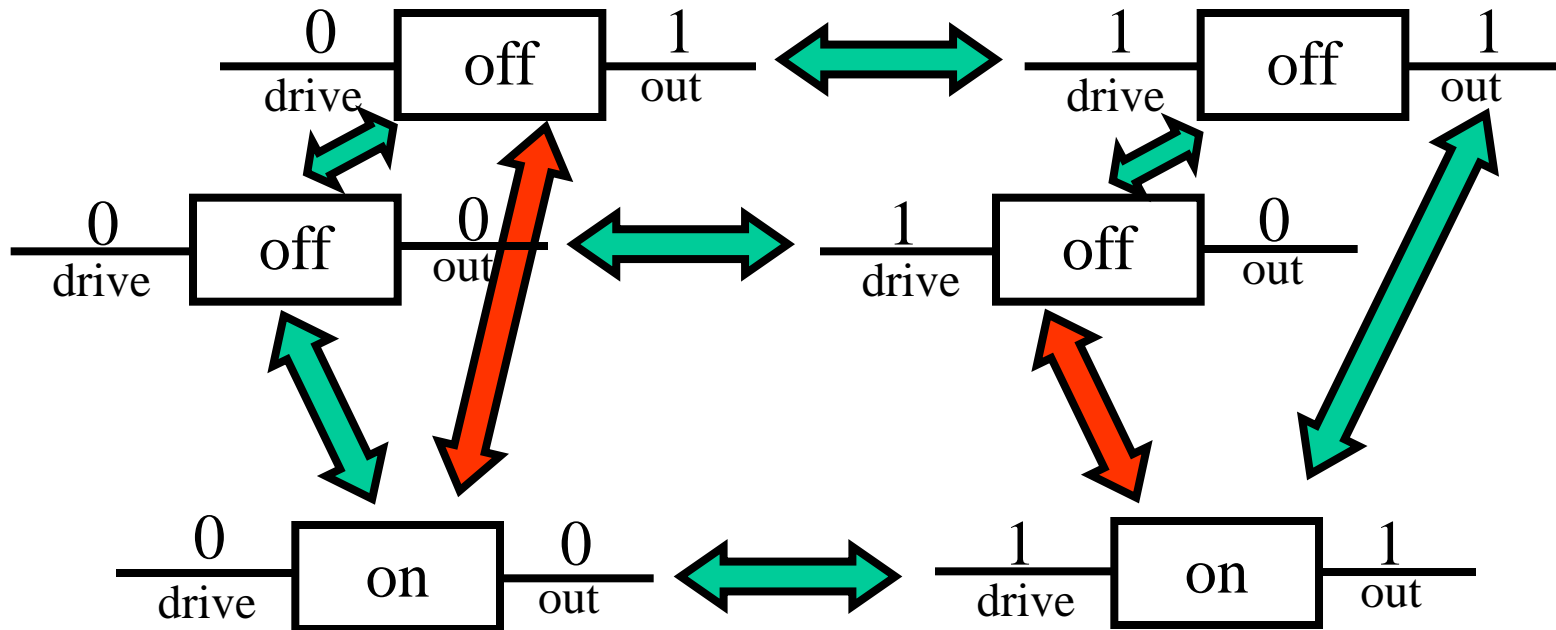
# Reversible & Irreversible T-gate Transitions


- When drive and gate are both data-dependent
  - Certain data transitions must be avoided...


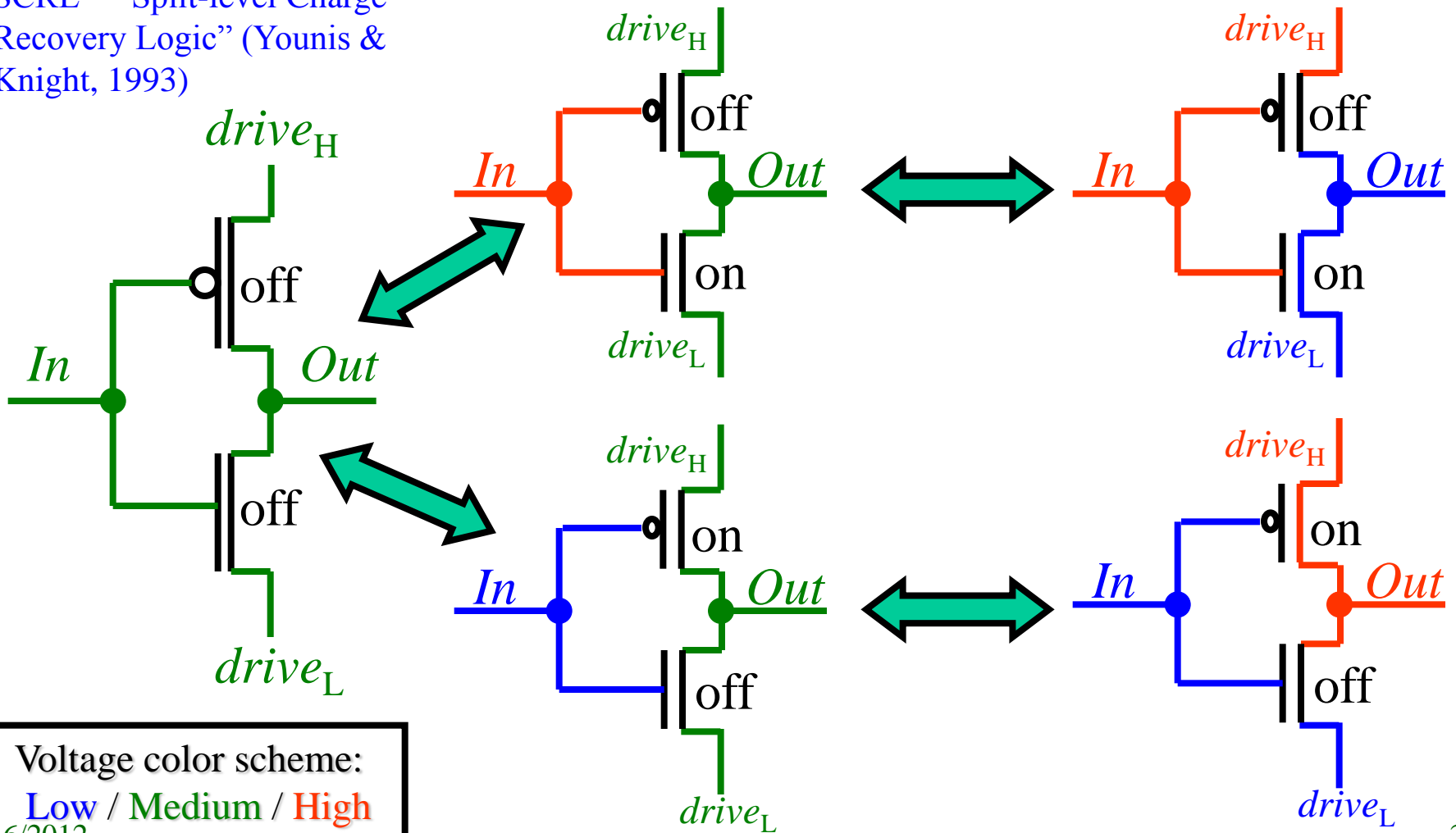
# Type 2 example: SCRL inverter (w/o latch)

- Same structure as static CMOS inverter, but used reversibly.
- Produces a fully-restored, amplified output signal.
- Inverters can be cascaded, but need latches to get feedback.

SCRL = "Split-level Charge Recovery Logic" (Younis & Knight, 1993)



Voltage color scheme:

Low / Medium / High

# SCRL Inverter Transition Table


Before SCRL-Inv		After SCRL-Inv	
<i>In</i>	<i>Out</i>	<i>In</i>	<i>Out</i>
0	0		
<b>0</b>	$\frac{1}{2}$	<b>0</b>	<b>1</b>
0	1		
$\frac{1}{2}$	0		
$\frac{1}{2}$	$\frac{1}{2}$		
$\frac{1}{2}$	1		
1	0		
<b>1</b>	$\frac{1}{2}$	<b>1</b>	<b>0</b>
1	1		

- Conditionally reversible, if input is valid and output is  $\frac{1}{2}$  just before drivers do their thing.
- No point in even listing the table entries that don't occur; can summarize operation below.

Before SCRL-Inv		After SCRL-Inv	
<i>In</i>	<i>Out</i>	<i>In</i>	<i>Out</i>
<b>0</b>	$\frac{1}{2}$	<b>0</b>	<b>1</b>
<b>1</b>	$\frac{1}{2}$	<b>1</b>	<b>0</b>
 
# Spacetime Diagram for SCRL Inverter


- Note that the notation shows that *Out* is being computed from *In* on a separate wire.
  - *In* is explicitly not being inverted “in place.”
- Wedge symbols show ongoing dependence.
  - Of course, we can always undo the op later.





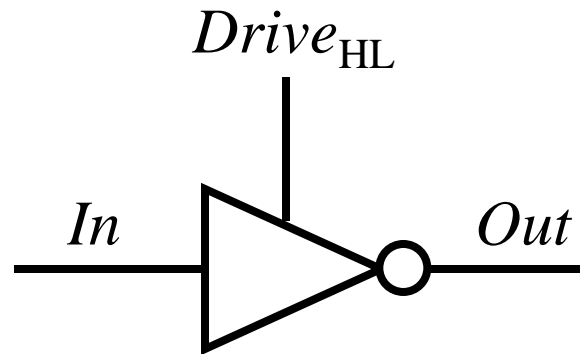
# Icon for SCRL Inverter

- Same as normal inverter icon
  - Can (optionally) also show control (drive) bus.



 - Note we can build a latched SCRL inverter very easily:




Internal node (might not be labeled)

# $rsCopyInv(In, Out)$

 
## Reversible Split-level Copy with Inversion

- Preconditions:
  - $Out$  is initially clear (logic N - neutral).
- Semantics:
  - $Out := \neg In$
- Gate icon in hardware diagrams:
  - (same gate also performs  $rUnCopyInv$ .)


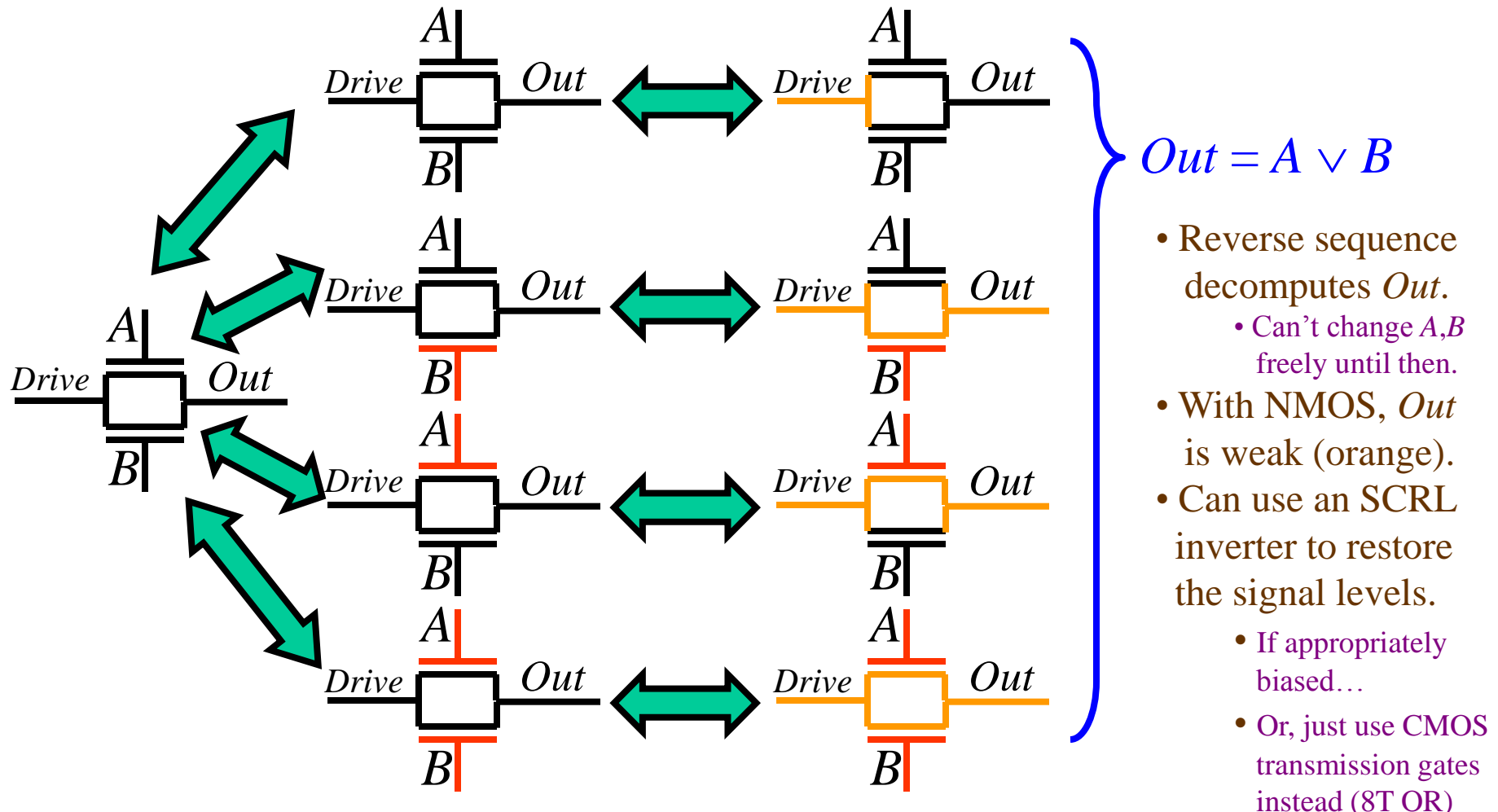
# Simple Logic Example: Adiabatic NMOS OR gate

- Input barriers along two parallel paths




# Type 3: Input-Barrier, Clocked-Bias Latching Logic

## ● Cycle of operation:

1. Input *conditionally lowers barrier*
  - Do logic w. series/parallel barriers
2. Clock applies bias force; conditional bit flip
3. Input removed, *raising the barrier & locking in the state-change*

4. Clock bias can retract



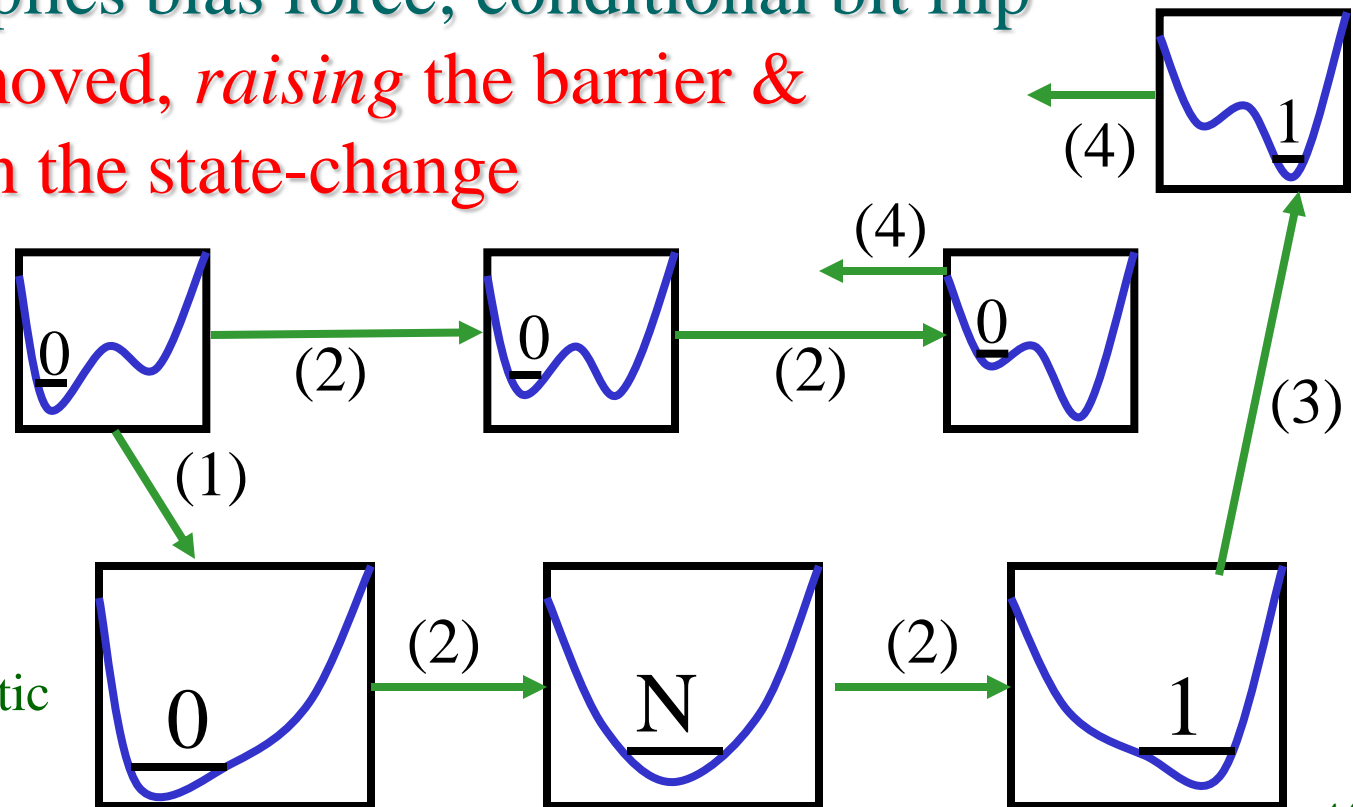


**Examples:** Mike's  
4-cycle 2-level adiabatic  
CMOS logic (2LAL)
  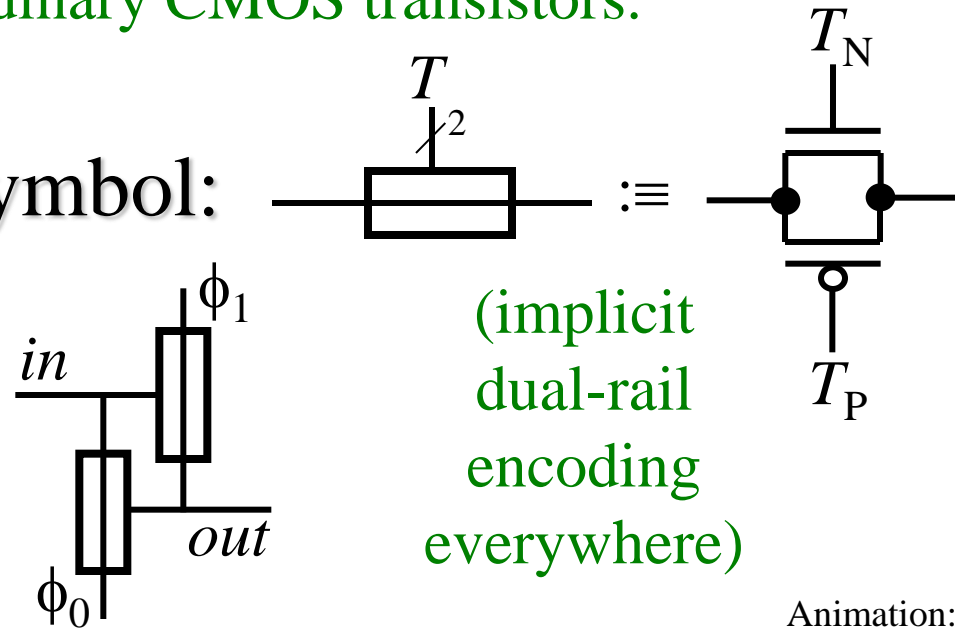
# 2LAL: 2-level Adiabatic Logic


A pipelined fully-adiabatic logic invented at UF (Spring 2000), implementable using ordinary CMOS transistors.

- Use simplified T-gate symbol:
- Basic buffer element:
  - cross-coupled T-gates:
    - need 8 transistors to buffer 1 dual-rail signal
- Only 4 timing signals  $\phi_{0-3}$  are needed. Only 4 ticks per cycle:
  - $\phi_i$  rises during ticks  $t \equiv i \pmod{4}$
  - $\phi_i$  falls during ticks  $t \equiv i+2 \pmod{4}$











Animation:  
  
 2lalswf

# 2LAL Cycle of Operation

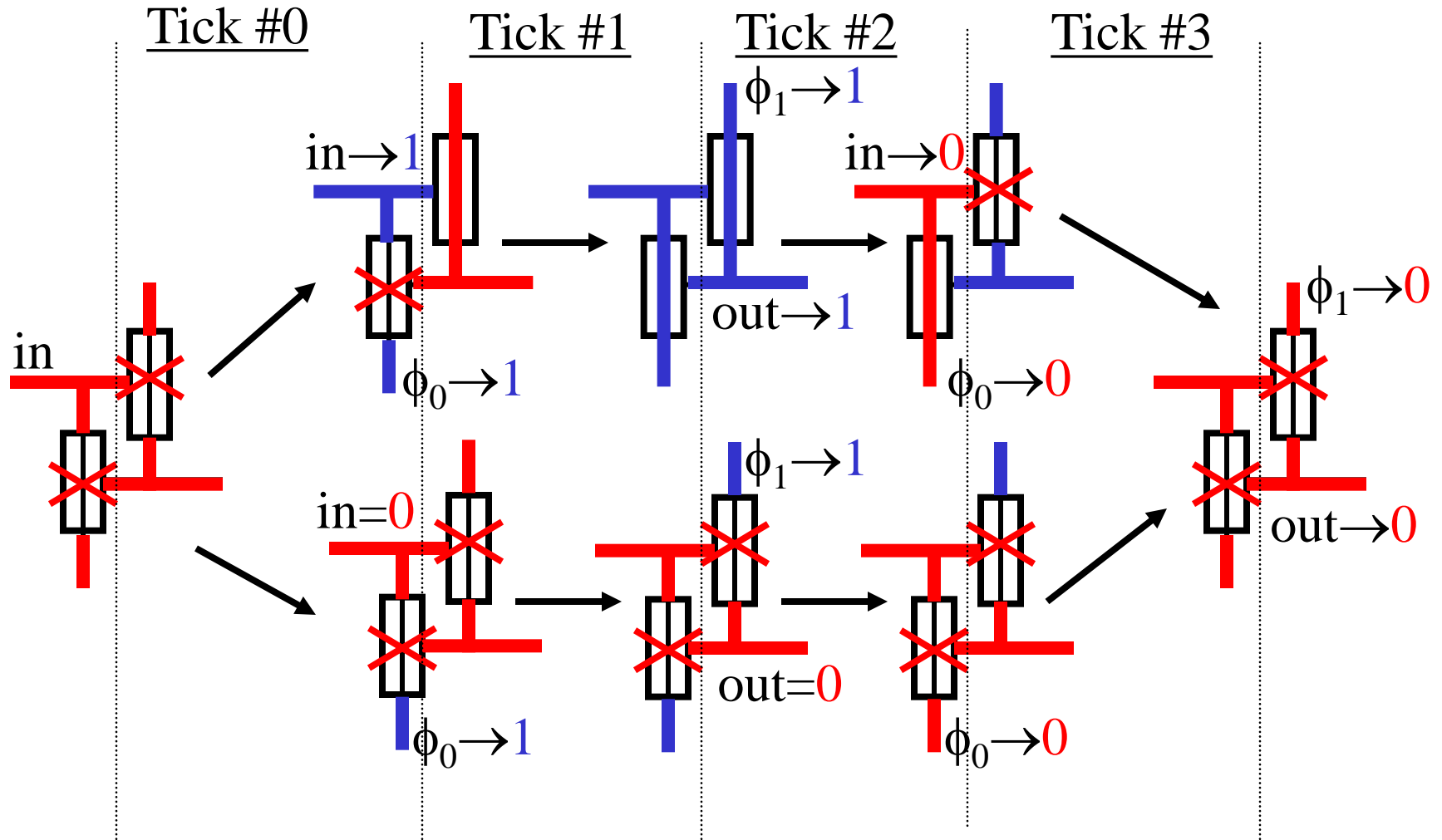

# A Schematic Notation for 2LAL

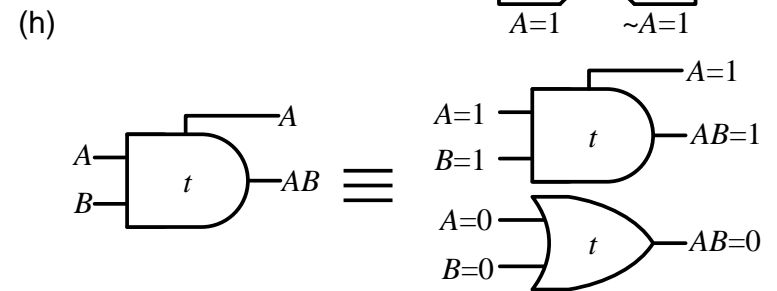       


# 2LAL Shift Register Structure


Animation:



- 1-tick delay per logic stage:

 

 
- Logic pulse timing and signal propagation:




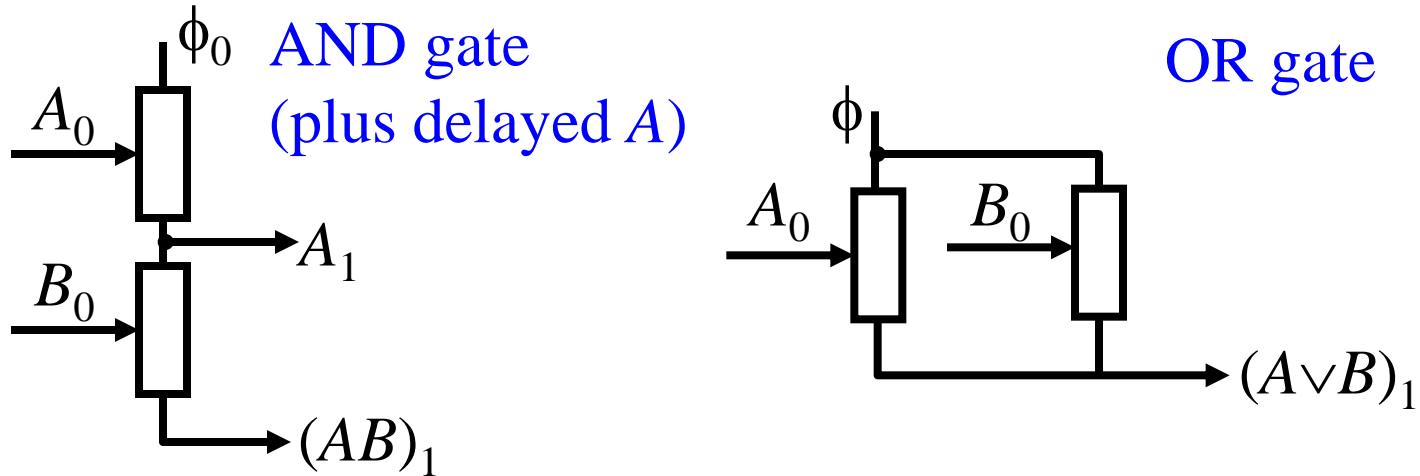
# More Complex Logic Functions


- Non-inverting multi-input Boolean functions:



- One way to do inverting functions in pipelined logic is to use a quad-rail logic encoding:


– To invert, just swap the rails!

- Zero-transistor “inverters.”

 
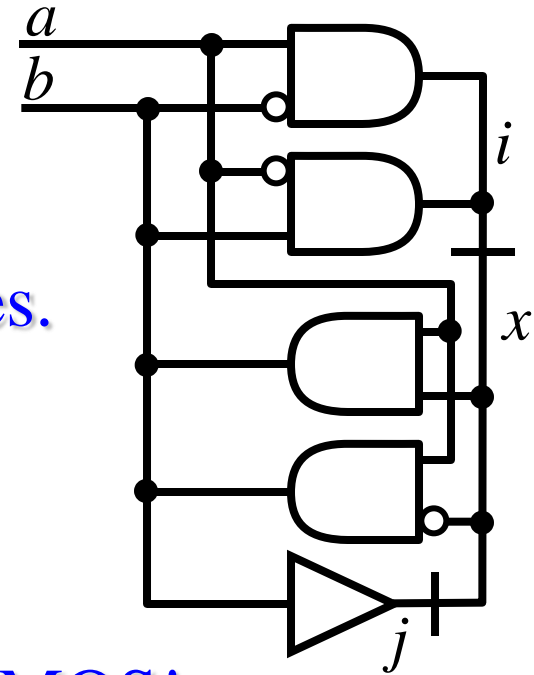
# cNOT hardware diagram

- Here is an implementation of in-place **cNOT**( $a,b$ ) (controlled-NOT)
  - In terms of reversible AND or OR, reversible buffers, reversible latches, and (0T dual-rail) complement bubbles.
- As you can see, it is rather complicated!
  - Illustrates that cNOT might not be a very good primitive for reversible CMOS!
- This structure can be properly called a **cNOT gate** (as opposed to a **cNOT operation**)



# cNOT operation sequence


- Steps to implement  $cNOT(a,b)$ :
 

	<u>a</u>	<u>b</u>	<u>i</u>	<u>x</u>	<u>j</u>
	a	b	0	0	0
1. rIXOR(a, b, x):					
1a. rUnLatch(i, x)	a	b	( 0 )	0	
1a. rAND(a, <u>b</u> , i), rAND( <u>a</u> , b, i)	a	b	(a⊕b)	0	
1b. rLatch(i, x)	a	b	a⊕b	a⊕b	0
1c. rUnAND(a, <u>b</u> , i), rUnAND( <u>a</u> , b, i)	a	b	0	a⊕b	0
2. rAND(a, x, b), rUnAND(a, <u>x</u> , b)	a	a⊕b	0	a⊕b	0
3. rUnCopy(b, x):					
3a. rcSET(b, j)	a	a⊕b	0	a⊕b	a⊕b
3b. rUnLatch(j, x)	a	a⊕b	0	(a⊕b)	
3c. rcUnSet(b, j)	a	a⊕b	0	( 0 )	
3d. rLatch(j, x)	a	a⊕b	0	0	0
- Note it takes 9 full steps!
 
# Shift Register Simulation Results (Cadence/Spectre)

Power vs. freq., TSMC 0.18, Std. CMOS vs. 2LAL

2LAL = Two-level adiabatic logic (invented at UF, '00)




- Graph shows power dissipation vs. frequency
  - in 8-stage shift register.
- At moderate frequencies (1 MHz),
  - Reversible uses  $< 1/100^{\text{th}}$  the power of irreversible!
- At ultra-low power (1 pW/transistor)
  - Reversible is 100× faster than irreversible!
- Minimum energy dissip. per nFET is  $< 1$  eV!
  - 500× lower than best irreversible!
    - 500× higher computational energy efficiency!
- Energy transferred is still  $\sim 10$  fJ ( $\sim 100$  keV)
  - So, energy recovery efficiency is 99.999%!
    - Not including losses in power supply, though

# $\Theta(\log n)$ -time Recursive Adiabatic Wired-OR Carry-Skip Adder

(8 bit segment shown)

With this recursive structure,  
we can do a  $2^n$ -bit add in  $2(n+1)$   
logic levels.

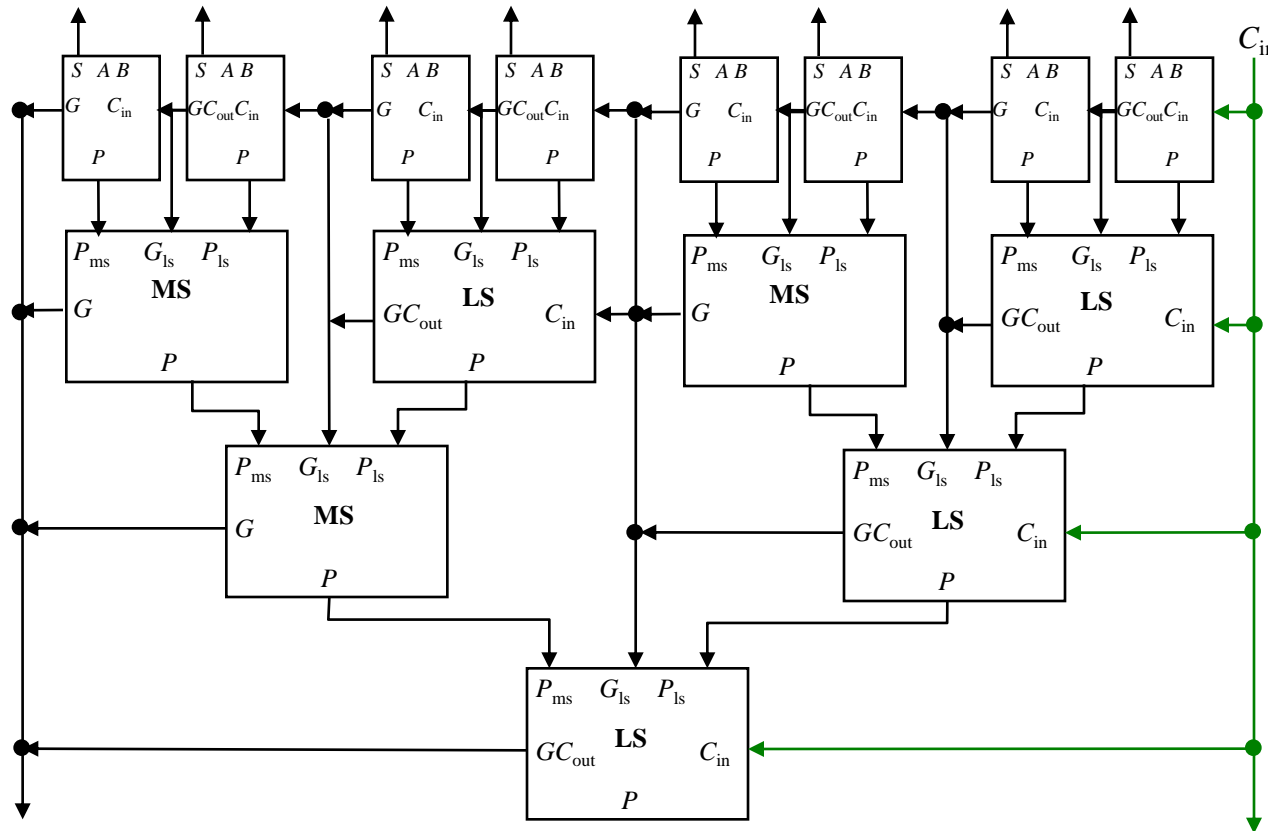
Hardware  
overhead is  
 $< 2 \times$  regular  
ripple-carry!




# 32-bit Adder Simulation Results

Further improvements may be attainable through more pipelining, carry-save adders, etc.

## 32-bit adder power vs. frequency

 

## 32-bit adder energy vs. frequency

 


(Results are normalized to a throughput level of 1 add/cycle)

# Reversible and/or Adiabatic Full-Custom VLSI Chips Designed @ MIT, 1996-1999


By EECS grad students Josie Ammer, Mike Frank, Nicole Love, Scott Rixner, and Carlin Vieri under CS/AI lab members Tom Knight and Norm Margolus.

Tick

 


First Fabbed CPU with a Reversible ISA

FlatTop

 

First Adiabatic FPGA

XRAM

 

First Adiabatic RAM

Pendulum



First Fully Adiabatic CPU

# Things to Do

- Explore whether this more-general paradigm for conditionally-reversible logic primitives might be helpful in developing reversible designs in technologies other than CMOS.
  - In particular, superconducting technologies.
    - May facilitate porting designs between domains.
- Build up a much more comprehensive variety of larger functional-unit designs based on this general approach.
  - And teach more designers how to work with it!